



MONTANA
STATE UNIVERSITY


Transistors & Logical Gates

...

Getting Down to The Metal


Hardware

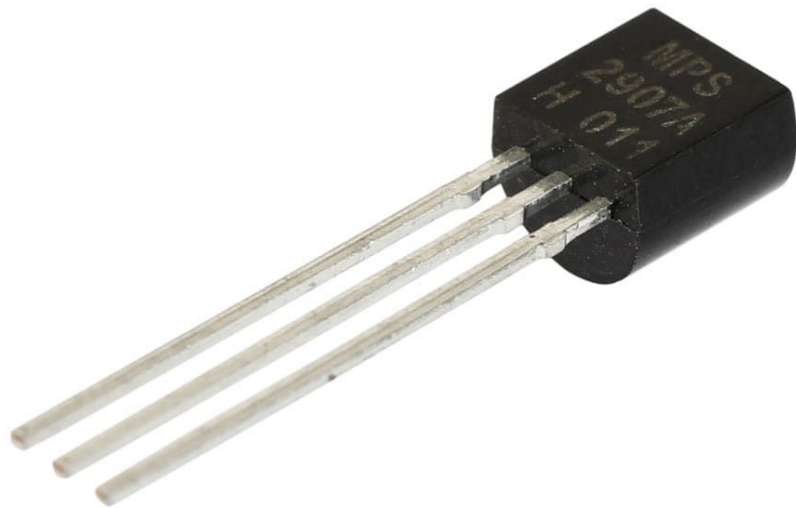- OK, it's time to get down to brass tacks
- We are going to look at how computers work at the physical level
- We will start by looking at *transistors*




Hardware

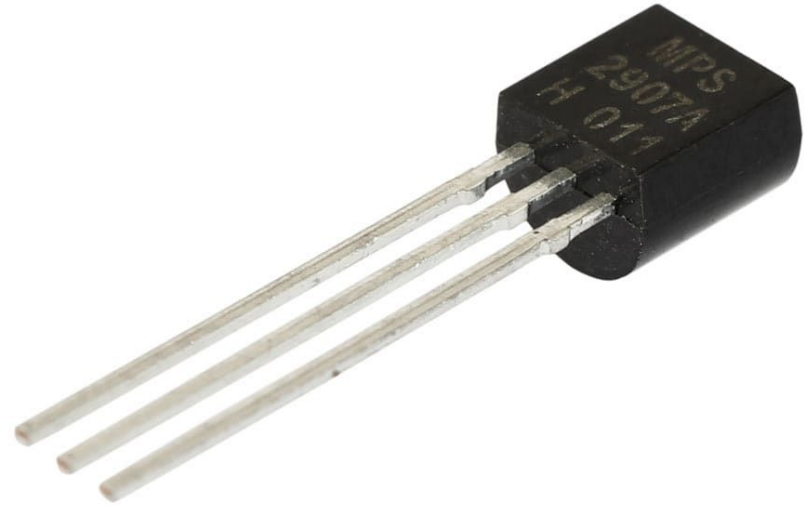- Note: I am not an electrical engineer
- I do not expect you to be an electrical engineer
- However, I do expect you to understand a bit about the underlying hardware in your computer



Transistors

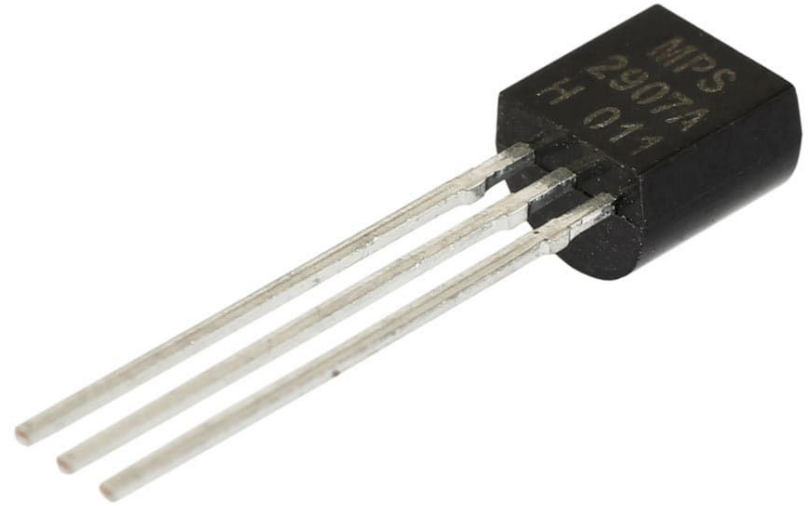- Pictured right is a *transistor*
- A transistor is semiconductor device that can be used to amplify or switch electronic signals
 - We will be concerned with switching, since we are discussing computer hardware



Transistor History

- Proposed in 1926 by Austrian Julius Lilienfeld
- First working transistor built at Bell Labs in 1947
 - John Bardeen
 - Walter Brattain
 - William Shockley




Transistor History

- Proposed in 1926 by Austrian Julius Lilienfeld
- First working transistor built at Bell Labs in 1947
 - John Bardeen
 - Walter Brattain
 - William Shockley




Transistor

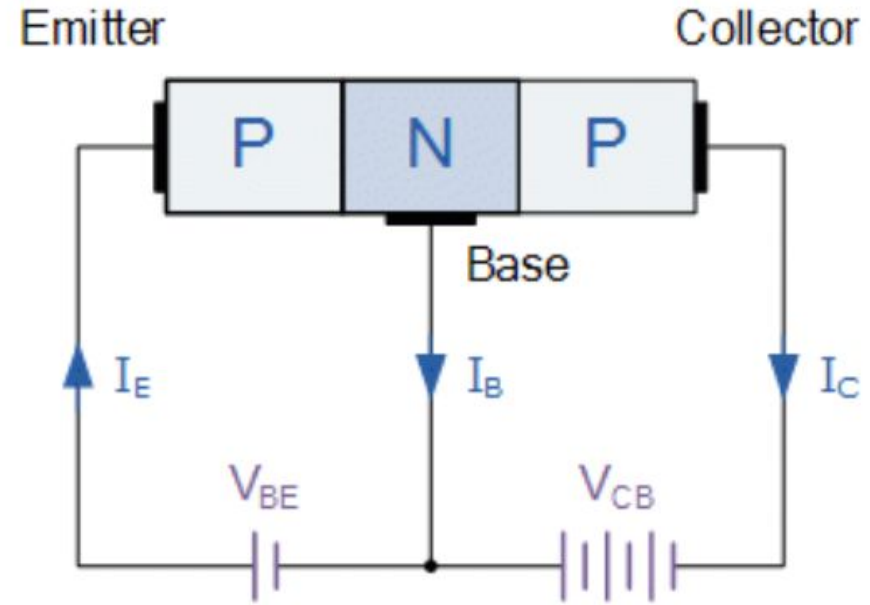- The Basic *Digital Transistor* Concept
 - Three input wires
 - Signal In 1 (Collector)
 - Signal In 2 (Base)
 - Signal Out (Emitter)
 - When a current is applied to the base wire, current will flow from the Collector to the Emitter wire
 - Or *not flow*, depending on the transistor type




Transistor

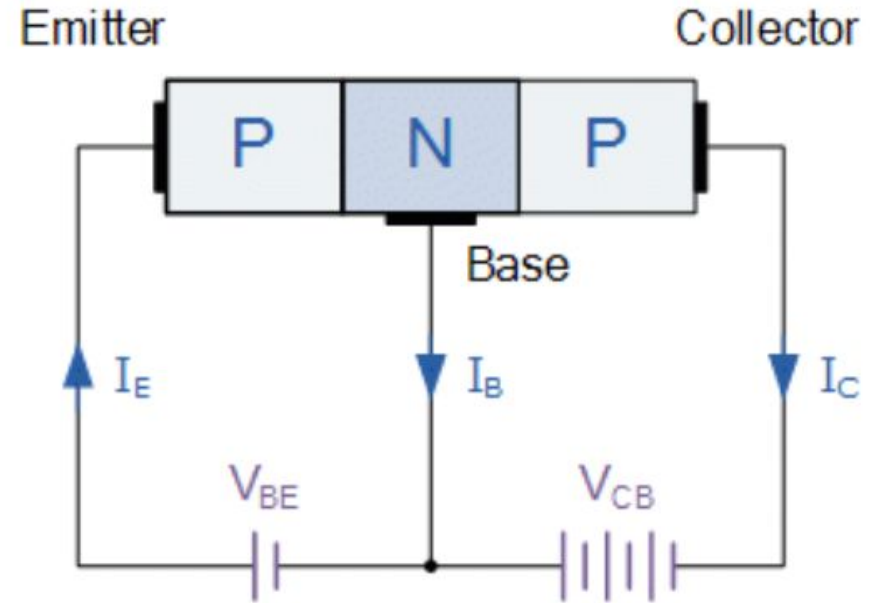- This is accomplished via materials engineering that makes the N region, picture here conductive when a signal is received from the base wire




Transistor History

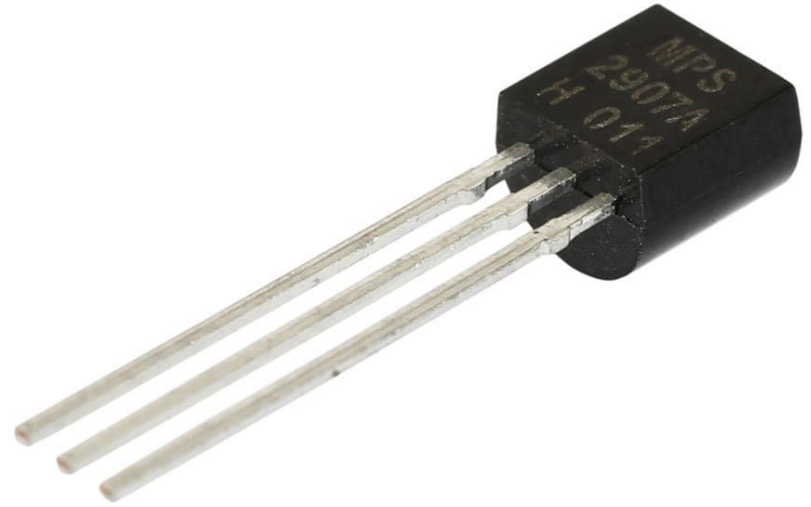- Transistors then can be used as the basis for building digital systems
 - High (or low) voltage indicates a 1
 - Low (or high) voltage indicates a 0



Logical Gates

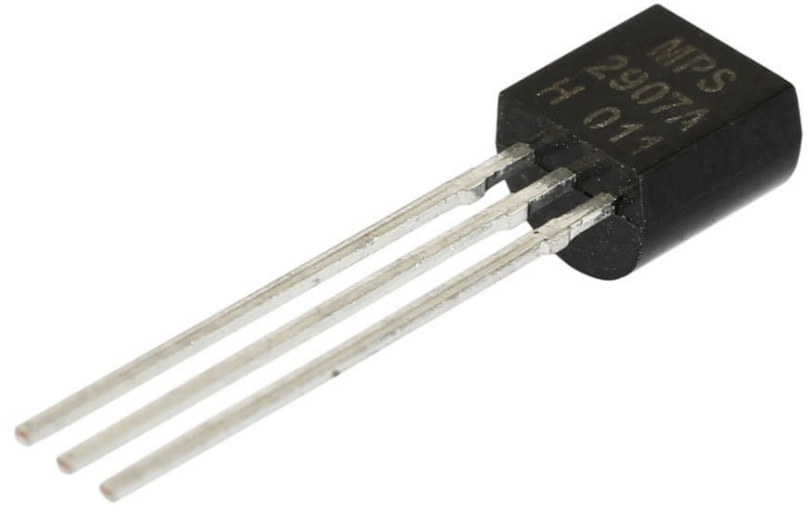- Using this idea we can create something called a *NAND gate*
- But first, let us review our logical operations and truth tables



AND

- By convention
 - 1 as high voltage = True
 - 0 as low voltage = False
- Recall the bitwise AND operator:

1 if A and B are both 1

A && B

A	B	(A \wedge B)
F	F	F
F	T	F
T	F	F
T	T	T

OR

- The bitwise OR operator:

1 if either A or B are 1

A		B
---	--	---

A	B	(A ∨ B)
F	F	F
F	T	T
T	F	T
T	T	T

NOT

- The bitwise NOT operator:

1 if A is 0

0 if A is 1

!A

A	$\neg A$
F	T
T	F

NAND

- The bitwise NOT AND operator:

1 if either A or B are 0

!A || !B

A	B	$(\neg A \vee \neg B)$
F	F	T
F	T	T
T	F	T
T	T	F

NAND


- NAND is very important
- It turns out that *all other logical operations* can be created using a NAND operator
 - This is also true of NOR
 - NAND and NOR are *functionally complete*
 - More on this gate type in a bit

!A		!B
----	--	----

A	B	$(\neg A \vee \neg B)$
F	F	T
F	T	T
T	F	T
T	T	F


Transistor Implementations

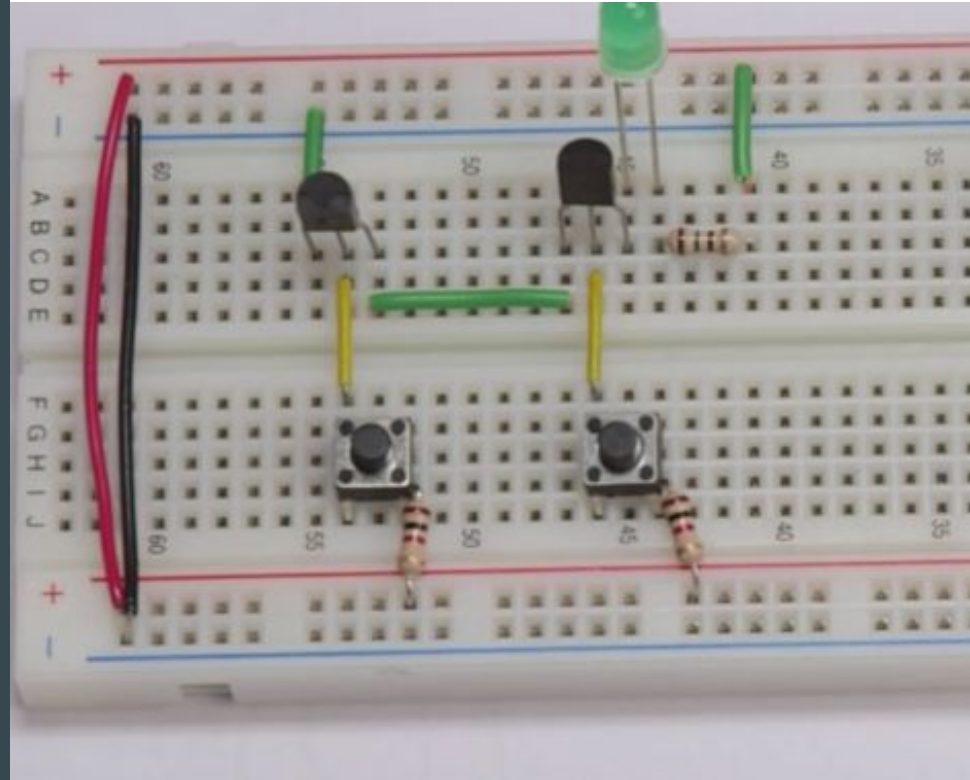- Using transistors, we can implement these logical operations
- Pictured right is a logical AND
- If both buttons are pressed, current will flow through the transistors
- This allows electricity to flow through the led, lighting it up







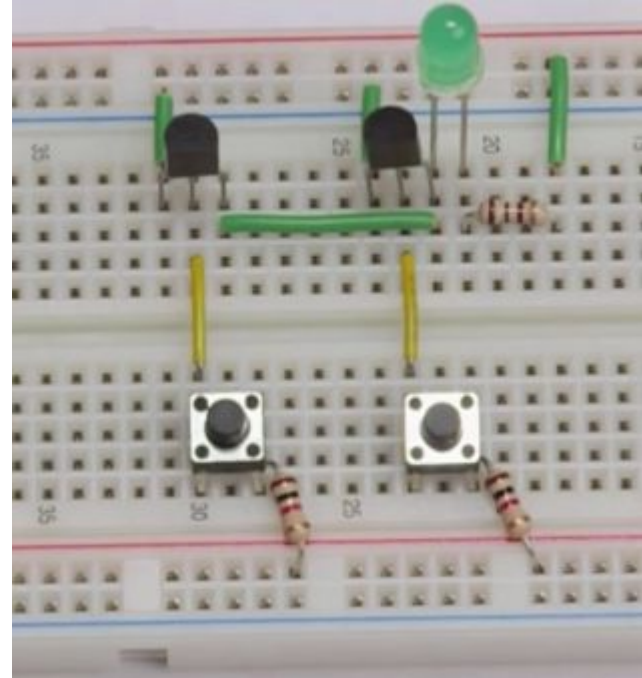


Transistor Implementations

- Here is an example of an OR
- If no button is pressed, no current is available to the LED
- If either button is pressed, current is available to the LED



Logical Symbols

- When designing digital systems, symbols are used for the various logical gates
 - NAND
 - OR
 - XOR
 - AND
 - NOT
 - NOT
 - XNOR

	NAND	Opposite of AND
	OR	Either is true (or both)
	XOR	Exactly one is true
	AND	Both are true
	NOT	Reverses the input
	NOR	Opposite of OR
	XNOR	Opposite of XOR

NAND Gate

- Recall that I said that NAND gates are special
 - NAND gates are functionally complete
 - All other gates can be constructed with them



$$Q = A \text{ NAND } B$$


Truth Table

Input A	Input B	Output Q
0	0	1
0	1	1
1	0	1
1	1	0

NOT Gate

- To create a NOT, simply put *both* inputs into a NAND

Desired NOT Gate

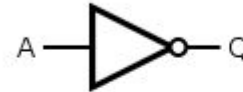

$$Q = \text{NOT}(A)$$

NAND Construction



$$= A \text{ NAND } A$$

Truth Table

Input A	Output Q
0	1
1	0

AND Gate


- AND gate construction
- Easy: NOT (A NAND B)

Desired AND Gate



$$Q = A \text{ AND } B$$

NAND Construction

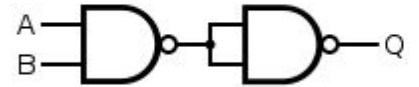

$$= (A \text{ NAND } B) \text{ NAND } (A \text{ NAND } B)$$

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	0
1	0	0
1	1	1

OR Gate


- A little more complicated
- (NOT A) NAND (NOT B)

Desired OR Gate



$$Q = A \text{ OR } B$$

NAND Construction

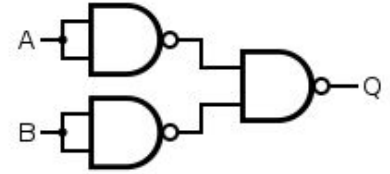


$$= (A \text{ NAND } A) \text{ NAND } (B \text{ NAND } B)$$

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	1

NPN vs PNP Transistors

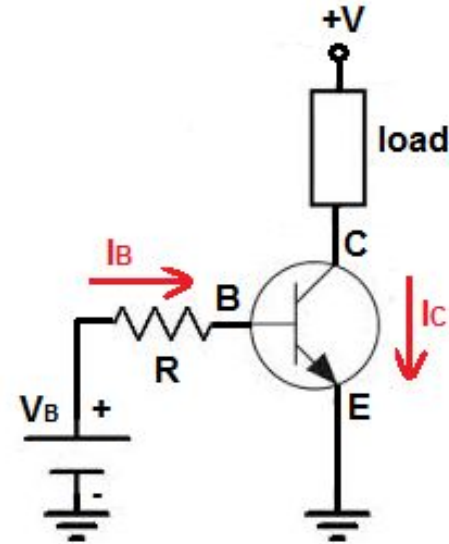
- It turns out there are two different major types of transistors
- NPN Transistors
 - Positive voltage allows current to flow
 - This is what we have been discussing mainly so far



In an NPN transistor, positive voltage is given to the collector terminal and current flows from the collector to the emitter, given there is sufficient base current

NPN vs PNP Transistors

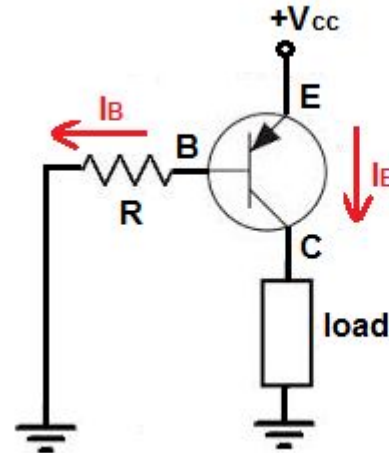
- PNP Transistors
 - Application of voltage *prevents* current from flowing
 - Inverts the logic of the NPN transistor



In a PNP transistor, positive voltage is given to the emitter terminal and current flows from the emitter to the collector, given there is sufficient negative current flow from the base


Field-Effect Transistors

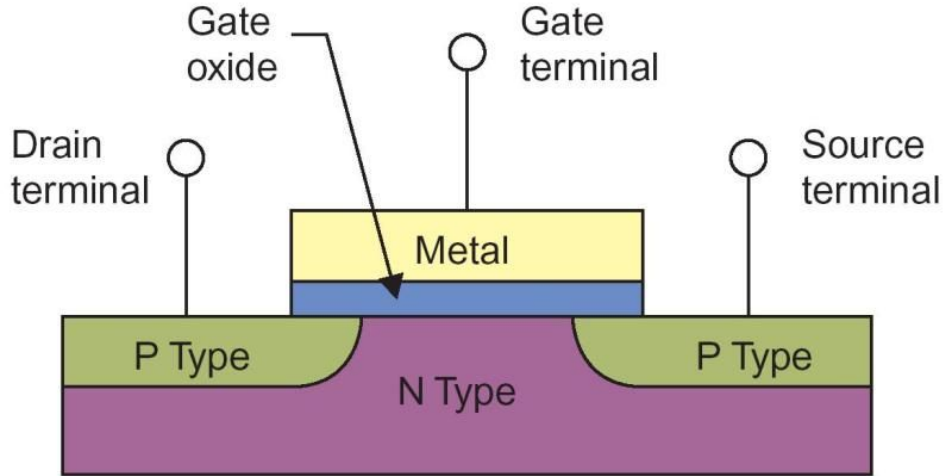- In order to make transistors smaller, our friends in EE have been creating smaller and smaller implementations of these basic building blocks
- MOSFET technology has been used to reduce and pack in transistors in mind bending amounts




Field-Effect Transistors

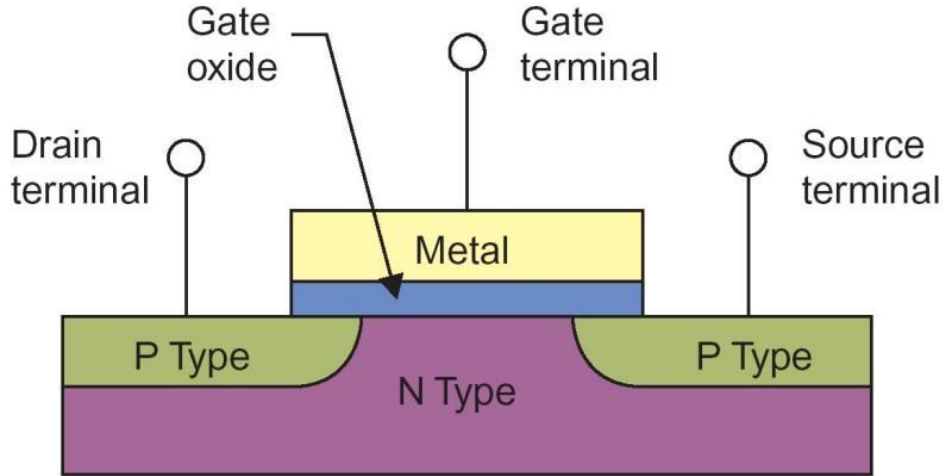- The NPN and PNP equivalent in MOSFETs are called NMOS and PMOS



NAND Gates & Transistors

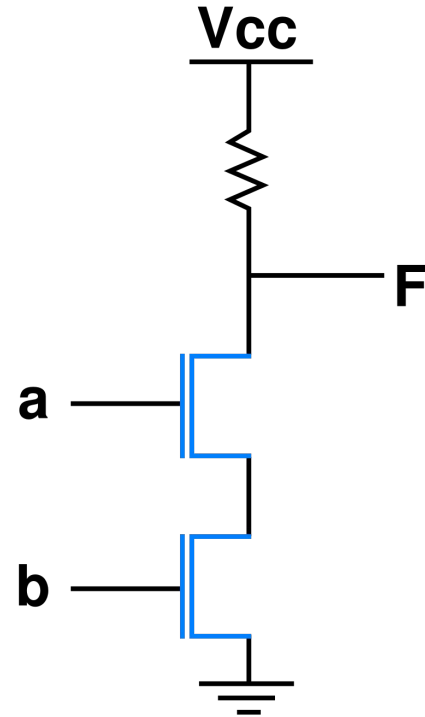
- How could we implement a NAND using NPN transistors?
- Here is the diagram for an NMOS NAND gate
 - If A and B are high, current will flow from Vcc to ground
 - Otherwise it will flow out (F)
- A simple NAND implementation!



**NMOS
NAND gate**


NAND Gates & Transistors

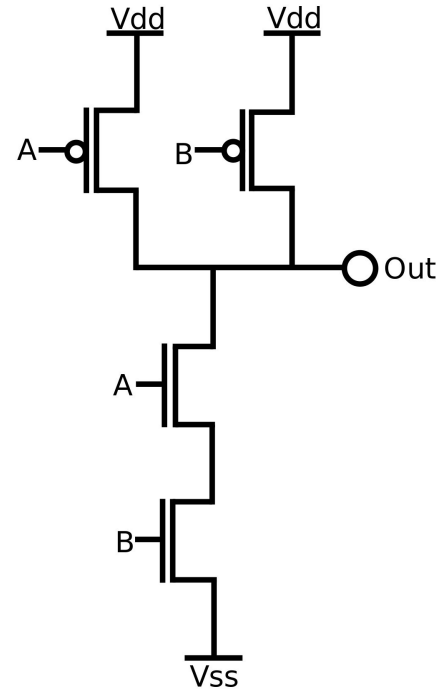- A more modern and slightly more complex CMOS NAND gate
- Note that the top transistors are PNP gates (thus voltage *stops* current) while the bottom gates are NPN transistors



NAND Gates & Transistors

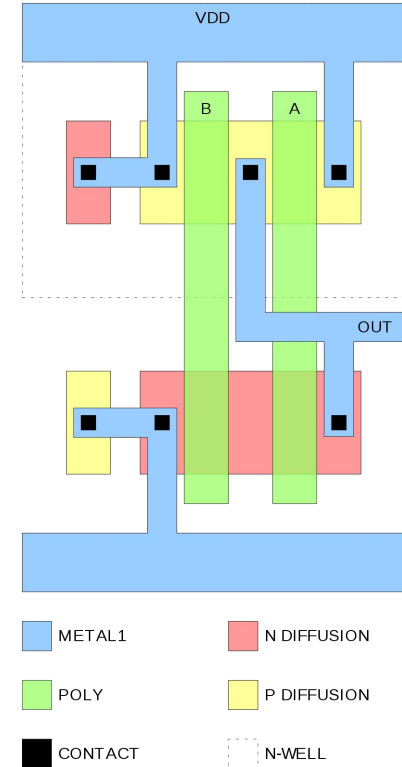- A physical layout of a NAND gate
- CMOS uses *both* NPN/NMOS and PNP/PMOS type semiconductors
 - Again, this is not an EE class
 - Just know that
 - NPN/NMOS - current flows if voltage is applied
 - PNP/PMOS - current flows if voltage is NOT applied



Transistors & Logical Gates

- Today took a beginners tour of the lowest level of digital computing
- We discussed transistors, an electrical device that can be used for digital switching
- We revisited the logical operators
 - We discussed how NAND can be used to create other logical operators
- We looked at how to implement these logical operators using transistors
- *REMEMBER: IT'S JUST LIGHTNING RUNNING THROUGH SAND*



MONTANA
STATE UNIVERSITY